

# Electronique numérique

## Initiation à VHDL (1/3)

### CORRECTIONS

1. Dessiner l'enveloppe externe du composant décrit par cette entité. [Voir figure 1.](#)
2. Dessiner l'entité d'un demi-additionneur, puis le code VHDL de cette entité. [Voir figure 4](#)
3. Rappeler la constitution interne du demi-additionneur. [Voir figure 4](#)
4. Coder l'architecture de ce demi-additionneur.

---

```
1 library ieee;
2 use ieee.std_logic_1164.all;
3
4 entity half_adder is
5     port(
6         a,b : in std_logic;
7         sum,cout : out std_logic
8     );
9 end half_adder;
10
11 architecture logic of half_adder is
12 begin
13     sum <= a xor b;
14     cout <= a and b;
15 end logic;
```

---

 


FIGURE 1 – Entity du composant MonCircuit

 


FIGURE 2 – Entité et architecture du demi-additionneur 1 bit

5. Dessinez la constitution interne d'un additionneur 1 bit complet, à partir du demi-additionneur.
6. Coder en VHDL l'architecture de cet additionneur 1 bit.

---

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity full_adder is
5      port(
6          a,b : in std_logic;
7          cin : in std_logic;
8          sum,cout : out std_logic
9      );
10 end full_adder;
11
12 architecture logic of full_adder is
13     signal s_1, cout_1,cout_2 : std_logic;
14 begin
15
16     ha_1 : entity work.half_adder(logic)
17     port map(
18         a => a,
19         b => b,
20         sum => s_1,
21         cout => cout_1
22     );
23
24     ha_2 : entity work.half_adder(logic)
25     port map(
26         a => cin,
27         b => s_1,
28         sum => sum,
29         cout => cout_2

```

 


FIGURE 3 – Architecture du demi-additionneur 1 bit

```

30 );
31
32 cout <= cout_1 or cout_2;
33
34 end logic;

```

#### 7. Coder en VHDL l'entité et l'architecture d'un additionneur 8 bits.

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity adder8b is
5    port(
6      a,b : in std_logic_vector(7 downto 0);
7      sum : out std_logic_vector(7 downto 0);
8      cout : out std_logic
9    );
10 end adder8b;
11
12 architecture structural of adder8b is
13   signal dummy_carry : std_logic;
14   signal carry : std_logic_vector(7 downto 0);
15 begin
16
17   dummy_carry <= '0';
18
19   fa_0 : entity work.full_adder(logic)
20   port map(

```

```

21     a => a(0),
22     b => b(0),
23     cin => dummy_carry,
24     sum => sum(0),
25     cout => carry(0)
26 );
27
28 fa_1 : entity work.full_adder(logic)
29 port map(
30     a => a(1),
31     b => b(1),
32     cin => carry(0),
33     sum => sum(1),
34     cout => carry(1)
35 );
36
37 fa_2 : entity work.full_adder(logic)
38 port map(
39     a => a(2),
40     b => b(2),
41     cin => carry(1),
42     sum => sum(2),
43     cout => carry(2)
44 );
45
46 fa_3 : entity work.full_adder(logic)
47 port map(
48     a => a(3),
49     b => b(3),
50     cin => carry(2),
51     sum => sum(3),
52     cout => carry(3)
53 );
54
55 fa_4 : entity work.full_adder(logic)
56 port map(
57     a => a(4),
58     b => b(4),
59     cin => carry(3),
60     sum => sum(4),
61     cout => carry(4)
62 );
63
64 fa_5 : entity work.full_adder(logic)
65 port map(
66     a => a(5),
67     b => b(5),
68     cin => carry(4),
69     sum => sum(5),

```

```

70     cout => carry(5)
71 );
72
73 fa_6 : entity work.full_adder(logic)
74 port map(
75     a => a(6),
76     b => b(6),
77     cin => carry(5),
78     sum => sum(6),
79     cout => carry(6)
80 );
81
82 fa_7 : entity work.full_adder(logic)
83 port map(
84     a => a(7),
85     b => b(7),
86     cin => carry(6),
87     sum => sum(7),
88     cout => carry(7)
89 );
90
91 cout <= carry(7);
92
93 end structural;

```

---

8. Le testbench présente également une entité. Localisez cette entité. En quoi est-elle particulière ? Comment peut-on l'expliquer ?  
 Un tel banc de test possède une entité *vide* : elle ne possède aucune entrée, ni sortie. C'est le laboratoire, portes closes.
9. Un générateur d'horloge est contenu dans le banc de test. Combien de lignes sont nécessaires ? Dessinez le chronogramme de cette horloge.  
 Une seule ligne suffit. On inverse le signal tous les demi-période d'horloge, à l'aide d'une assignation conditionnée par un signal "running", qui nous permettra de contrôler l'arrêt de la simulation
10. Comment notre banc de test provoque t-il concrètement cet arrêt ? Le signal running est affecté à "false" à la fin du processus de stimulation. Plus aucun événement n'est créé par le simulateur.
11. Dessiner le chronogramme des stimuli.
12. L'additionneur fonctionne-t-il avec des nombres signés ? Oui ! En tous les cas, un test semble aller en ce sens ! Voir figure ??.

## 1 Script de compilation

Script de compilation GHDL (donné sous Moodle) :

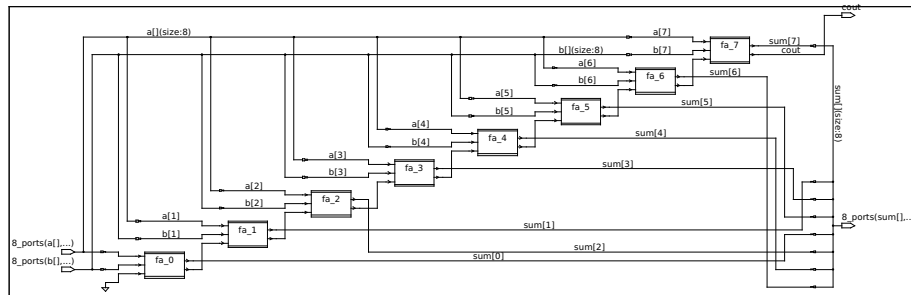


FIGURE 4 – Architecture de l'additionneur 8 bits

 


FIGURE 5 – Chronogramme (overview)

 


FIGURE 6 – Chronogramme : cas de  $1 + 255$

 


FIGURE 7 – L'additionneur fonctionne pour les nombres signés.

```

echo "=> cleaning..."
rm -rf waves.ghw *.o
echo "=> analyzing VHDL files..."
ghdl -a half_adder.vhd
ghdl -a full_adder.vhd
ghdl -a adder8b.vhd
ghdl -a adder8b_tb.vhd
echo "=> elaboration..."
ghdl -e adder8b_tb
echo "=> running simulation"
ghdl -r adder8b_tb --wave=waves.ghw
echo "=> starting waveform viewer"
gtkwave waves.ghw chrono.sav

```

Testbench (donné sous Moodle) :

```

1  -----
2  -- This file was generated automatically by vhd_ltb Ruby utility
3  -- date : (d/m/y) 05/11/2018 15:40
4  -- Author : Jean-Christophe Le Lann - 2014
5  -----
6  library ieee;
7  use ieee.std_logic_1164.all;
8  use ieee.numeric_std.all;
9
10 entity adder8b_tb is
11 end entity;
12
13 architecture bhv of adder8b_tb is
14
15     constant HALF_PERIOD : time := 5 ns;
16
17     signal clk : std_logic := '0';
18     signal reset_n : std_logic := '0';
19     signal sreset : std_logic := '0';
20     signal running : boolean := true;
21
22     procedure wait_cycles(n : natural) is
23     begin
24         for i in 1 to n loop
25             wait until rising_edge(clk);
26         end loop;
27     end procedure;
28
29     signal a : std_logic_vector(7 downto 0);
30     signal b : std_logic_vector(7 downto 0);
31     signal sum : std_logic_vector(7 downto 0);
32     signal cout : std_logic;
33

```



```

34 begin
35 -----
36 -- clock and reset
37 -----
38 reset_n <= '0','1' after 666 ns;
39
40 clk <= not(clk) after HALF.PERIOD when running else clk;
41
42 -----
43 -- Design Under Test
44 -----
45 dut : entity work.adder8b(using_generate)
46
47     port map (
48         a => a ,
49         b => b ,
50         sum => sum ,
51         cout => cout
52     );
53
54 -----
55 -- sequential stimuli
56 -----
57 stim : process
58     variable expected_sum : signed(7 downto 0);
59     variable nb_errors : natural := 0;
60     function str(v : std_logic_vector(7 downto 0)) return String is
61     begin
62         return integer'image(to_integer(unsigned(v)));
63     end ;
64
65 begin
66     a <= (others=>'0');
67     b <= (others=>'0');
68     report "running testbench for adder8b(structural)";
69     report "waiting for asynchronous reset";
70     wait until reset_n='1';
71     wait_cycles(10);
72     report "applying stimuli...";
73     for i in 0 to 255 loop
74         for j in 0 to 255 loop
75             wait until rising_edge(clk);
76             a <= std_logic_vector(to_unsigned(i,8));
77             b <= std_logic_vector(to_unsigned(j,8));
78             expected_sum := signed(a)+signed(b);
79             if expected_sum /= signed(sum) then
80                 report "ERROR for sum : " & str(a) & "+" & str(b);
81                 report "expecting " & str(std_logic_vector(expected_sum)) & ". Got " & str(sum);
82                 nb_errors:=nb_errors+1;

```

```

83         else
84             report "OK for sum : " & str(a) & "+" & str(b);
85         end if;
86     end loop;
87 end loop;
88
89 wait_cycles(100);
90 a <= std_logic_vector(to_signed(45,8));
91 b <= std_logic_vector(to_signed(-48,8));
92 wait_cycles(100);
93 report "end of simulation";
94 report "number of errors detected : " & integer'image(nb_errors);
95 running <= false;
96 wait;
97 end process;
98
99 end bhv;

```

---

## 2 Using generate

---

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  architecture using_generate of adder8b is
5      signal dummy_carry : std_logic;
6      signal carry : std_logic_vector(7 downto 0);
7  begin
8
9      dummy_carry <= '0';
10
11     Loop_index: for i in 0 to 7 generate
12
13         first_stage: if i=0 generate
14             stage_0: entity work.full_adder(logic)
15                 port map(
16                     a => a(i),
17                     b => b(i),
18                     cin => dummy_carry,
19                     sum => sum(i),
20                     cout => carry(i)
21                 );
22         end generate;
23
24     other_stages: if i>0 generate
25         state_i: entity work.full_adder(logic)
26             port map(
27                 a => a(i),

```

```
28         b => b(i),
29         cin => carry(i-1),
30         sum => sum(i),
31         cout => carry(i)
32     );
33     end generate;
34
35 end generate;
36
37 cout <= carry(7);
38
39 end using_generate;
```

---